

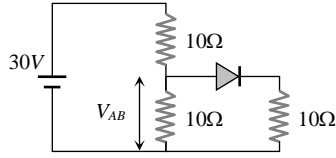


1. Find  $V_{AB}$

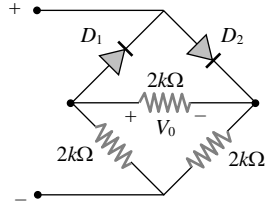- (a) 10 V
- (b) 20 V
- (c) 30 V
- (d) None of these



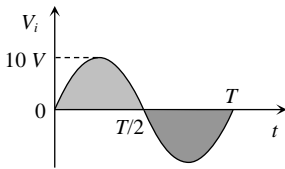
2. In the circuit shown in figure the maximum output voltage  $V_0$  is



- (a) 0 V
- (b) 5 V
- (c) 10 V
- (d)  $\frac{5}{\sqrt{2}}$  V


3. The following configuration of gate is equivalent to

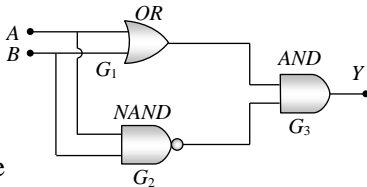- (a) NAND
- (b) XOR
- (c) OR
- (d) None of these



4. The diagram of a logic circuit is given below. The output  $F$  of the circuit is represented by

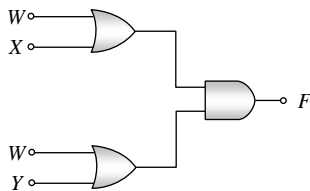- (a)  $W \cdot (X + Y)$
- (b)  $W \cdot (X \cdot Y)$
- (c)  $W + (X \cdot Y)$
- (d)  $W + (X + Y)$



5. The relation between  $I_p$  and  $V_p$  for a triode is

$$I_p = (0.125 V_p - 7.5) \text{mA}$$

Keeping the grid potential constant at 1V, the value of  $r_p$  will be


- (a) 8 kΩ
- (b) 4 kΩ
- (c) 2 kΩ
- (d) 8 kΩ

6. A triode whose mutual conductance is 2.5 mA/volt and anode resistance is 20 kilo ohm, is used as an amplifier whose amplification is 10. The resistance connected in plate circuit will be

- (a) 1 kΩ
- (b) 5 kΩ
- (c) 10 kΩ
- (d) 20 kΩ

7. The slopes of anode and mutual characteristics of a triode are  $0.02 \text{ mA V}^{-1}$  and  $1 \text{ mA V}^{-1}$  respectively. What is the amplification factor of the valve
- (a) 5                                      (b) 50  
 (c) 500                                    (d) 0.5

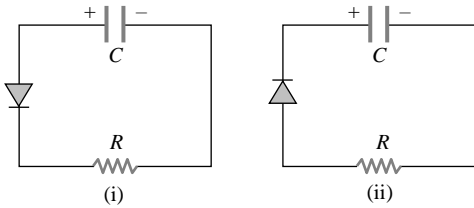
8. Two identical capacitors  $A$  and  $B$  are charged to the same potential  $V$  and are connected in two circuits at  $t = 0$ , as shown in figure. The charge on the capacitors at time  $t = CR$  are respectively



- (a)  $VC, VC$                               (b)  $\frac{VC}{e}, VC$   
 (c)  $VC, \frac{VC}{e}$                             (d)  $\frac{VC}{e}, \frac{VC}{e}$

9. In the following common emitter circuit if  $\beta = 100$ ,  $V_{CE} = 7V$ ,  $V_{BE} = \text{Negligible}$   $R_C = 2 \text{ k}\Omega$  then  $I_B = ?$

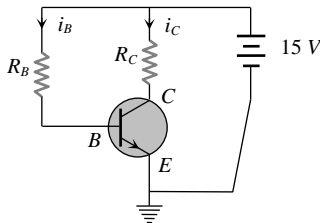
- (a)  $0.01 \text{ mA}$   
 (b)  $0.04 \text{ mA}$   
 (c)  $0.02 \text{ mA}$   
 (d)  $0.03 \text{ mA}$



10. Mobility of electrons in a semiconductor is defined as the ratio drift velocity to the applied electric field. If, for an n-type semiconductor, the density of electrons is  $10^{19} \text{ m}^{-3}$  and their mobility is  $1.6 \text{ m}^2 / (\text{V}\cdot\text{s})$  then the resistivity of the semiconductor (since it is an n-type semiconductor contribution of holes is ignored) is close to:


- (a)  $2 \Omega\text{m}$                                   (b)  $4 \Omega\text{m}$   
 (c)  $0.4 \Omega\text{m}$                                 (d)  $0.2 \Omega\text{m}$

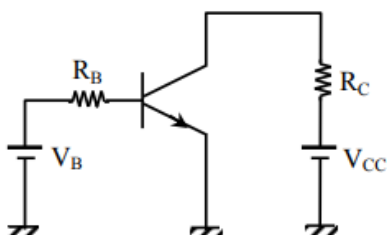11. A common emitter amplifier circuit, built using an npn transistor, is shown in figure. Its dc current gain is 250,  $R_C = 1 \text{ k}\Omega$  and  $V_{CC} = 10 \text{ V}$ . What is the minimum base current for  $V_{CE}$  to reach saturation ?






- (a)  $40 \mu\text{A}$                                     (b)  $100 \mu\text{A}$   
 (c)  $7 \mu\text{A}$                                       (d)  $10 \mu\text{A}$

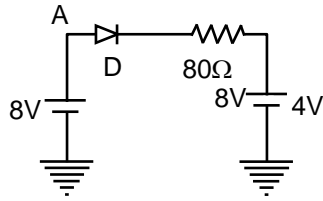12. The resistance of the given diode in F.B. condition is  $20\ \Omega$  and in R.B. condition it is  $2500\ \Omega$  the current in the circuit is :-



- (a) 20 mA                      (b) 40 mA  
 (c) 50 mA                      (d) 10 mA

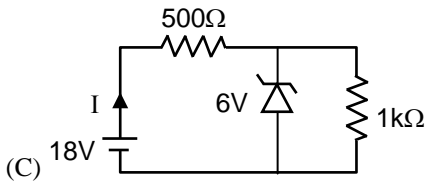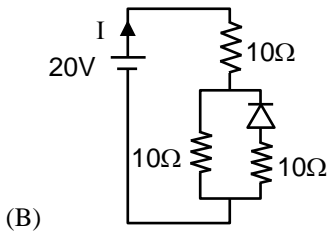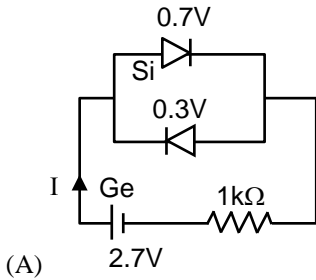13. What is the value of current I in given circuits :-



- (a) 2mA, 1A, 24mA                      (b) 2.4mA, 1.33A, 30mA  
 (c) 1.6 mA, 0.66A, 20mA                      (d) None

14. An amplifier is nothing but an oscillator with –

- (a) positive feedback                      (b) high gain  
 (c) no feed back                      (d) negative feed back

15. In the case of constants  $\alpha$  and  $\beta$  of a transistor

- (a)  $\alpha = \beta$                       (b)  $\beta < 1$   $\alpha > 1$   
 (c)  $\alpha\beta = 1$                       (d)  $\beta > 1$   $\alpha < 1$


16. For a common emmitter circuit if  $\frac{I_c}{I_E} = 0.98$  then current gain for common emitter circuit will be :

- (a) 49                      (b) 98  
 (c) 4.9                      (d) 25.5

17. A n-p-n transistor conducts when

- (a) both collector and emitter are positive with respect to the base
- (b) collector is positive and emitter is negative with respect to the base
- (c) collector is positive and emitter is at same potential as the base
- (d) both collector and emitter are negative with respect to the base

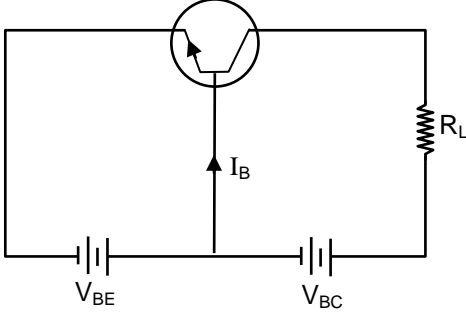18. In a common-base configuration of transistor.  $\alpha = 0.98$ ,  $I_B = 0.02 \text{ mA}$ ,  $R_L = 5 \text{ k}\Omega$ . Output voltage across load is :



- (a) 3.2 V
- (b) 4.9 V
- (c) 5.2 V
- (d) 6.2 V

19. In a common emitter amplifier using output resistance of 5000 ohm and input resistance of 2000 ohm, if the peak value of input signal voltage is 10 mV and  $\beta = 50$  then the calculated power gain will be

- (a)  $6.25 \times 10^3$
- (b) 1.4
- (c) 62.5
- (d)  $2.5 \times 10^4$


20. A transistor is operated in common emitter configuration at constant collector voltage  $V_c = 1.5 \text{ V}$  such that a change in the base current from  $100 \mu\text{A}$  to  $150 \mu\text{A}$  produces a change in the collector current from 5 mA to 10 mA. The current gain ( $\beta$ ) is :-

- (a) 67
- (b) 75
- (c) 100
- (d) 50

21. In a common base amplifier, the phase difference between the input signal voltage and output voltage is :

- (a)  $\frac{\pi}{4}$
- (b)  $\pi$
- (c) zero
- (d)  $\frac{\pi}{2}$

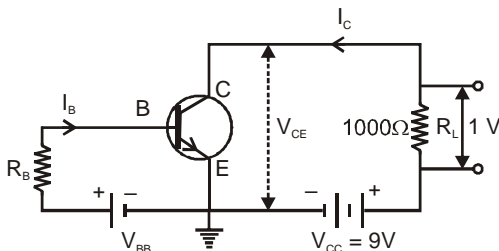
22. An N-P-N transistor is connected in common emitter configuration in which collector supply is 9V and the voltage drop across the load resistance of  $1000\Omega$  connected in the collector circuit is 1 V. If current amplification factor is  $(25/26)$ , If the internal resistance of the transistor is  $200\Omega$ , then which of the following options is **incorrect**.



- (a)  $V_{CE} = 8 \text{ V}$


- (b) collector current is 1.0 mA  
(c) voltage gain  $\frac{50}{23}$ , and power gain is 4.6  
(d) emitter current is 2.04 mA
23. The A-C current gain of a transistor is  $\beta = 19$ . In its common-emitter configuration, What will be the change in the emitter current for a change of 0.4 mA in the base-current ?  
(a) 7.6 mA      (b) 7.2 mA  
(c) 8 mA      (d) 6.8 mA
24. In a common emitter n-p-n transistor circuit, it is found that ninety percent of emitted electrons reach the collector. If the collector current is 18 mA then  
(a) Base current is 2 mA  
(b) Emitter current is 20 mA  
(c) Emitter current is 22 mA  
(d) Both (a) & (b)
25. A 6 volt battery is connected to the terminals of a three metre long wire of uniform thickness and resistance of 100 ohm. The difference of potential between two points on the wire separated by a distance of 50 cm will be -  
(a) 2 volt    (b) 3 volt    (c) 1 volt    (d) 1.5 volt
26. A standard cell of 1.08 V is balanced by the p.d. across 90 cms of a meter long wire supplied by a cell of emf 2V through a series resistor of resistance 2  $\Omega$ . If the internal resistance of cell in primary circuit is zero then the resistance per unit length of potentiometer wire is :  
(a) 3 ohm/cm      (b) 0.3 ohm/cm  
(c) 3 ohm/m      (d) 3 ohm/mm
27. If a semiconductor has an intrinsic carrier concentration of  $1.41 \times 10^{16} \text{ m}^{-3}$ , when doped with  $10^{21} \text{ m}^{-3}$  phosphorus, then the concentration of holes at room temperature will be -  
(a)  $2 \times 10^{21}$     (b)  $2 \times 10^{11}$     (c)  $1.41 \times 10^{10}$     (d)  $1.41 \times 10^{16}$
28. For a transistor working as common base amplifier, the emitter current is 7.2 mA. The current gain is 0.96. The collector current is -  
(a)  $0.96 \times 7.2 \text{ mA}$       (b)  $\frac{0.96}{0.72} \text{ mA}$   
(c)  $0.96 - 7.2 \text{ mA}$       (d)  $7.2 \text{ A} - 2 \times 0.96 \text{ mA}$
29. Given  $\beta = 80$  and  $\Delta I_B = 250 \mu\text{A}$ . The value of  $\Delta I_C$  is -  
(a)  $80 \times 250 \mu\text{A}$       (b)  $(250 - 80) \mu\text{A}$   
(c)  $(250 + 80) \mu\text{A}$       (d)  $\frac{250}{80} \mu\text{A}$
30. Knee voltage in Ge diode is of the order of -  
(a) 0.3 V    (b) 0.7 V    (c) 5 V    (d) 100 V

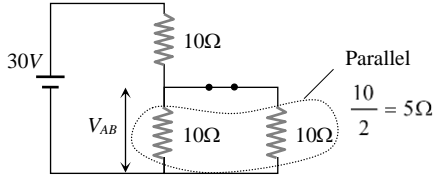1. (a) Diode is in forwards biasing hence the circuit can be redrawn as follows




$$V_{AB} = \frac{30}{(10 + 5)} \times 5 = 10 \text{ V}$$

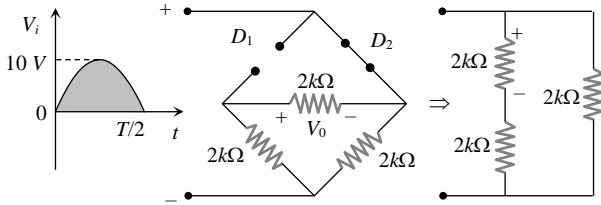2. (b) For the positive half cycle of input the resulting network is shown below



$$\Rightarrow (V_0)_{\max} = \frac{1}{2}(V_i)_{\max} = \frac{1}{2} \times 10 = 5 \text{ V.}$$

3. (b)

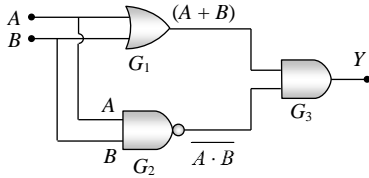

$$Y = (A + B). \overline{A \cdot B}$$

The given output equation can also be written as

$$Y = (A + B).(\overline{A} + \overline{B}) \quad (\text{De Morgan's theorem})$$

$$= A\overline{A} + A\overline{B} + B\overline{A} + B\overline{B} = 0 + A\overline{B} + \overline{A}B + 0 = \overline{A}B + A\overline{B}$$

This is the expression for XOR gate.

4. (c) Output of upper OR gate =  $W + X$

Output of lower OR gate =  $W + Y$

Net output  $F = (W + X)(W + Y)$

$$= WW + WY + XW + XY \quad (\text{Since } WW = W)$$

$$= W(1 + Y) + XW + XY \quad (\text{Since } 1 + Y = 1)$$

$$= W + XW + XY = W(1 + X) + XY = W + XY$$

5. (d)  $i_p = [0.125 V_p - 7.5] \times 10^{-3} \text{ amp}$

Differentiating this equation w.r.t.  $V_p$

$$\frac{\Delta i_p}{\Delta V_p} = 0.125 \times 10^{-3} \text{ or } \frac{1}{r_p} = 0.125 \times 10^{-3} \Rightarrow r_p = 8 \text{ k}\Omega$$

6. (b)  $\mu = r_p \times g_m = 20 \times 2.5 = 50$

$$\text{From } A = \frac{\mu R_L}{r_p + R_L} \Rightarrow r_p + R_L = \frac{\mu R_L}{A} = \frac{50 R_L}{10} = 5 R_L$$

$$\Rightarrow 4 R_L = r_p \Rightarrow R_L = \frac{r_p}{4} = \frac{20}{4} = 5 \text{ k}\Omega$$

7. (b) The slope of anode characteristic curve =  $\frac{1}{r_p}$

$$\Rightarrow r_p = \frac{1}{0.02 \text{ mA/V}} = 50 \frac{\text{V}}{\text{mA}} = 50 \times 10^3 \frac{\text{V}}{\text{A}}$$

The slope of mutual characteristic curve =  $g_m$

$$= 1 \times 10^{-3} \text{ A/V.}$$

$$\therefore \mu = r_p \times g_m = 50 \times 10^3 \times 10^{-3} = 50 .$$

8. (b) Time  $t = CR$  is known as time constant. It is time in which charge on the capacitor decreases to  $\frac{1}{e}$  times of its initial charge (steady state charge).

In figure (i)  $PN$  junction diode is in forward bias, so current will flow the circuit *i.e.*, charge on the capacitor decrease and in time  $t$  it becomes  $Q = \frac{1}{e}(Q_o)$ ; where  $Q_o = CV \Rightarrow Q = \frac{CV}{e}$

In figure (ii)  $P-N$  junction diode is in reverse bias, so no current will flow through the circuit hence change on capacitor will not decay and it remains same *i.e.*  $CV$  after time  $t$ .

9. (b)  $V = V_{CE} + I_C R_L$

$$\Rightarrow 15 = 7 + I_C \times 2 \times 10^3 \Rightarrow i_C = 4 \text{ mA}$$

$$\therefore \beta = \frac{i_C}{i_B} \Rightarrow i_B = \frac{4}{100} = 0.04 \text{ mA}$$

### 10. (c) JEE Main 2019

As we know, current density,

$$j = \sigma E = nev_d$$

$$\sigma = ne \frac{v_d}{E} = ne\mu$$

$$\frac{1}{\sigma} = \rho = \frac{1}{ne\mu_e} = \text{Resistivity}$$

$$= \frac{1}{10^{19} \times 1.6 \times 10^{19} - 19 \times 1.6}$$

or  $P = 0.4 \Omega m$

### 11. (a) JEE Main 2019

Given,  $\beta = 250$

$$\text{Voltage gain, } \frac{V_{CC}}{V_B} = \beta \frac{R_C}{R_B}$$

$$\frac{10}{V_B} = 250 \times \frac{10^3}{R_B}$$

$$\therefore \frac{V_B}{R_B} = \frac{1}{25 \times 10^3} = 40 \mu A$$

12. (b)

$$13. (a)(A) I = \frac{2.7 \times 0.7}{1 \times 10^3} = 2 \text{mA}$$

$$(B) I = \frac{20}{10 + 10} = 1 \text{A}$$

$$(C) I = \frac{18 - 6}{500} = 24 \text{mA}$$

14. (a)

15. (d)  $\alpha$  is the ratio of collector current and emitter current while  $\beta$  is the ratio of collector current and base current.

16. (a)

17. (b)

$$18. (b) \beta = \frac{\alpha}{1 - \alpha} = \frac{0.98}{1 - 0.98} = 49$$

$$\beta = \frac{I_C}{I_B} \Rightarrow I_C = \beta I_B = 49 \times 0.02 \text{ mA} = 0.98 \text{ mA}$$

$$V_{\text{Load}} = I_C R_L = (0.98 \text{ mA}) [5 \text{K}\Omega] = 4.9 \text{ volt}$$

19. (a) Power gain = current gain x voltage gain

$$\text{Voltage gain} = \beta \frac{R_{\text{out}}}{R_{\text{in}}} = \frac{5}{2} \times 50$$

$$\text{so. Power gain} = 50 \times 50 \times \frac{5}{2} = \frac{12500}{2} = 6250$$

20. (c)

21. (c)

22. (c)

23. (c) By definition, the A-C current gain  $\beta$  is given by

$$\beta_{\text{ac}} = \frac{\Delta I_C}{\Delta I_B}$$

$$\therefore \Delta I_C = \beta \times \Delta I_B = 19 \times 0.4 \text{ mA} = 7.6 \text{ mA.}$$


The emitter - current is the sum of the base- current and the collector-current ( $i_E = i_B + i_C$ )

$$\therefore \Delta I_E = \Delta I_B + \Delta I_C = 0.4 \text{ mA} + 7.6 \text{ mA} = 8 \text{ mA.}$$

24. (d)

25. (c)

$$V_{AB} = E$$

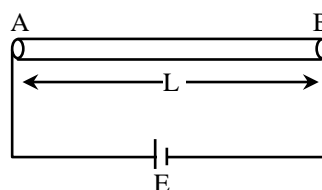



$$\text{Potential gradient } K = \frac{V_{AB}}{L} = \frac{E}{L}$$

$\therefore$  Potential difference across length  $\ell$  is  $V = K\ell$

$$= \frac{E}{L} \times \ell = \frac{6}{3} \times 0.5 = 1 \text{ volt}$$

26. (c)

$$E = \left( \frac{E_0}{L} \times \frac{R_w}{R_w + r + R_h} \right) \times \ell \quad (\because r = 0, R_h = 2 \Omega)$$

$$\therefore 1.08 = \left( \frac{2}{1\text{m}} \times \frac{R_w}{R_w + 2} \right) \times 0.90 \text{ m}$$

$$\frac{1.08}{2 \times 0.90} = \frac{R_w}{R_w + 2}$$

$$\text{Hence : } 0.6 = \frac{R_w}{R_w + 2}$$

$$0.6 R_w + 1.2 = R_w \Rightarrow 1.2 = 0.4 R_w \Rightarrow 3 = R_w$$

$\therefore$  Resistance per unit length is  $3\Omega/\text{meter}$

27. (d)

Phosphorus is pentavalent impurity. Its doping will not effect the concentration of holes. So number of holes will be equal to same as in intrinsic semiconductor. So  $n_h = 1.41 \times 10^{16} \text{ m}^{-3}$

28. (a)

$$\alpha = \frac{i_C}{i_E}$$

$$i_C = \alpha i_E = 0.96 \times 7.2 \text{ mA}$$

29. (a)

$$\Delta i_e = \beta \Delta i_B = 80 \times 250 \mu\text{A}$$

30. (b)

Theory